

# Determining the Transients and Steady State Charging Current and Voltage for RL Circuit

**Doug Patrick and Robert Ragan**


*Electrical and Computer Engineering*

*April 25, 2009*

Advisor: Professor Kin P. Moy

**Youngstown**  
STATE UNIVERSITY

*Choose Ohio First Cohorts*

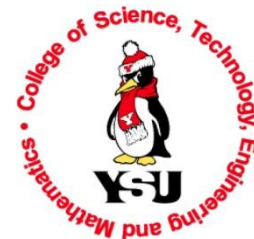

## Purpose

### *To develop time domain mathematical equation for charging current in a series $RL$ circuit using Laplace Transform*

- Develop of equations for transient current and voltage equations requires the use of differential equations (Time Domain)
- Typically beyond the mathematical capability of Freshmen engineering students
- Utilization of Laplace transformation (Frequency domain) would enable the solution to be obtained using only algebra


## Terms and Definitions

- **Transients** –  
A short-lived oscillation/decay in a system caused by a sudden change of voltage or current expressed as a function of time exponentially
- **Inductor-**  
An electrical device (typically a conducting coil) that introduces inductance (stored current ) into a circuit
- **Steady State-**  
A condition of a physical system or device that does not change over time
- **Laplace Transform-**  
A mathematical technique to enable solution of Differential Equations utilizing algebra via transformation between time and frequency domain

## RL Circuit Elements


- **Voltage Source -  $E$  (Volts)**
- **Resistor -  $R$  (Ohms)**
- **Inductor –  $L$  (Henry)**
- **Inductor Current –  $I_L$  (Ampere)**
- **Inductor Voltage -  $V_L$  (Volts)**
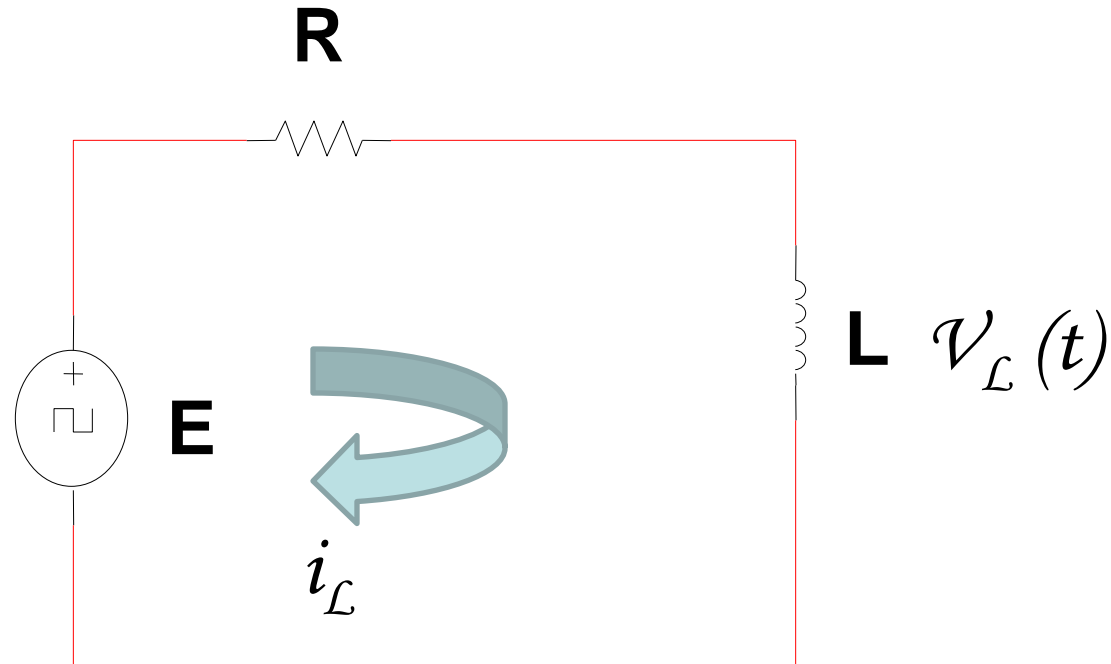
# RL Circuit - Time Domain Differential Equation



$$iR + L \frac{di}{dt} = E \quad (\text{Kirchhoff' Voltage Law})$$
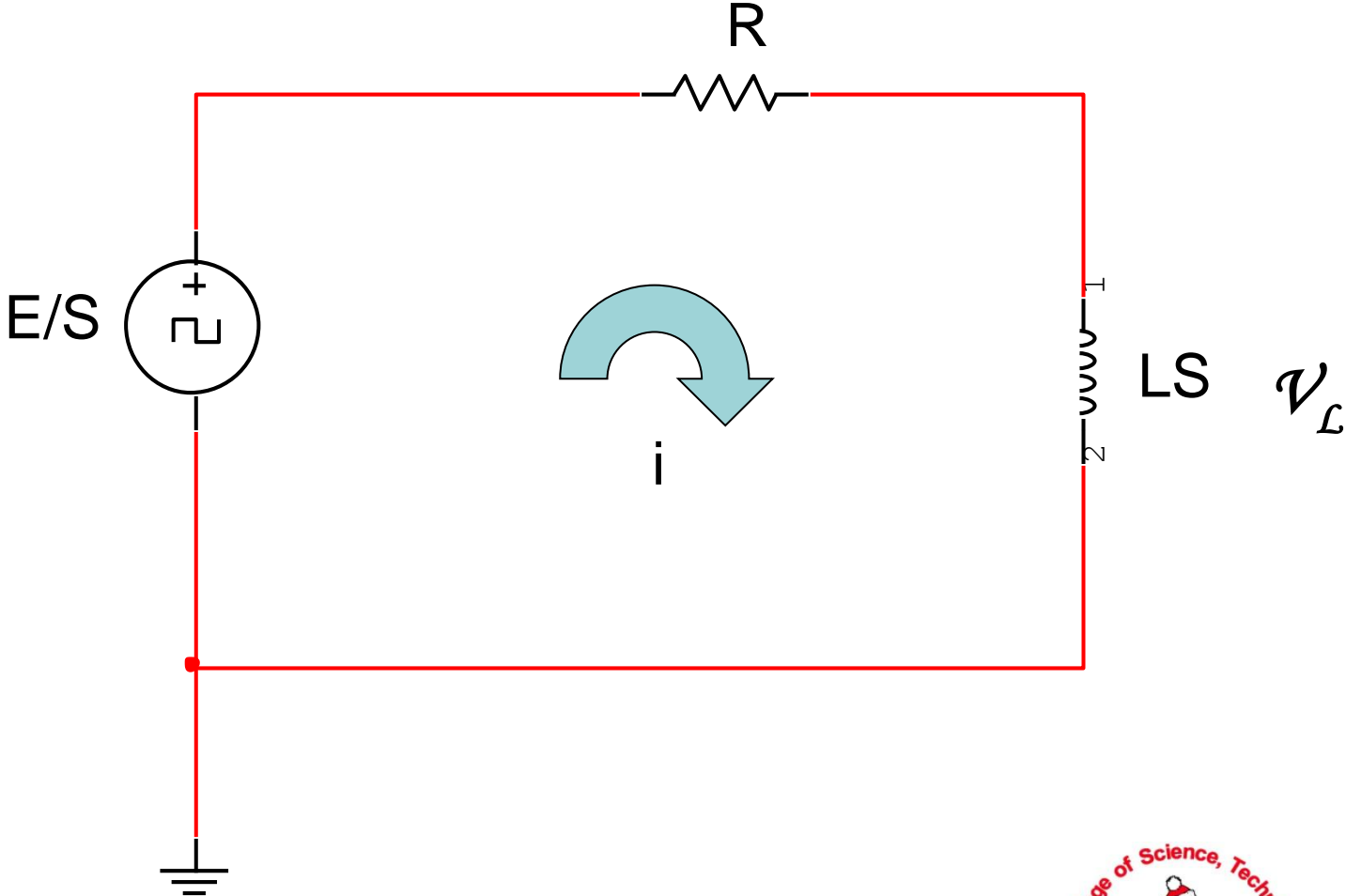
# Laplace Transform (Frequency Domain) Circuit



## Transient Current Equation - Laplace Transform (Frequency Domain)

$$\begin{aligned} I(s) &= \frac{\frac{E}{s}}{R + Ls} = \frac{E}{(s)(R + Ls)} \\ &= \left(\frac{E}{L}\right) \frac{1}{s \left(s + \frac{1}{\tau}\right)} \end{aligned}$$

*Applying Partial Fraction*

$$= \frac{E}{L} \left( \frac{A}{s} + \frac{B}{s + \frac{1}{\tau}} \right)$$

$$\text{Where } \tau = \frac{L}{R}$$

## Transient Current Frequency/Time Domain Transformation

$$I(S) = \frac{E}{R} \left[ \frac{1}{S} - \frac{1}{S + \frac{1}{\tau}} \right] \quad a = 1/\tau$$

*By applying inverse Laplace Transform Properties*

$$\mathcal{L}^{-1} \left( \frac{E}{S} \right) = E \quad \mathcal{L}^{-1} \left( \frac{1}{(S + a)} \right) = e^{-\frac{t}{\tau}}$$

*The Frequency Domain equation can be transformed into Time Domain equation*

$$i(t) = \frac{E}{R} \left( 1 - e^{-\frac{t}{\tau}} \right)$$

## Charging Voltage - Frequency Domain Equation

Applying voltage divider, the inductor voltage is:

$$\mathcal{V}_L = \frac{E}{S} \left( \frac{LS}{R+LS} \right)$$

After simplifications:

$$\mathcal{V}_L = \frac{E}{S + \frac{R}{L}} = E \left( \frac{1}{S + 1/\tau} \right)$$

Time constant  $\tau = L/R$

## Transient Voltage Frequency/Time Domain Transformation

*Applying Inverse Laplace Transform Property :*


$$\mathcal{L}^{-1} \left( \frac{1}{(S + a)} \right) = e^{-\frac{t}{\tau}} \quad a = 1/\tau$$

*The time domain equation is*

$$V_L = E e^{-t/\tau}$$


# Transient Current Time Domain Waveform – Excel

## Transient Charging Current - Inductor

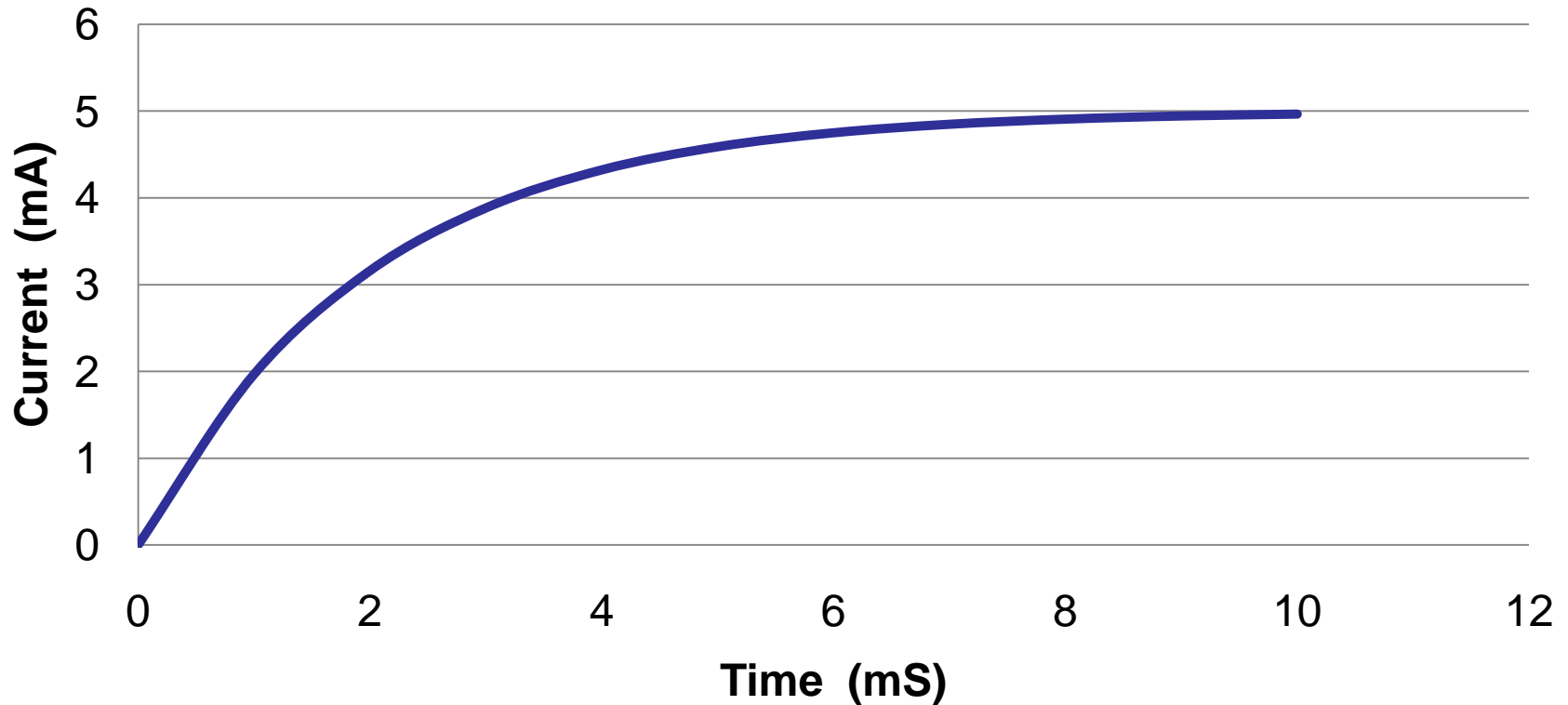


# Transient Voltage Time Domain Waveform – Excel


## Transient Charging Voltage - Inductor

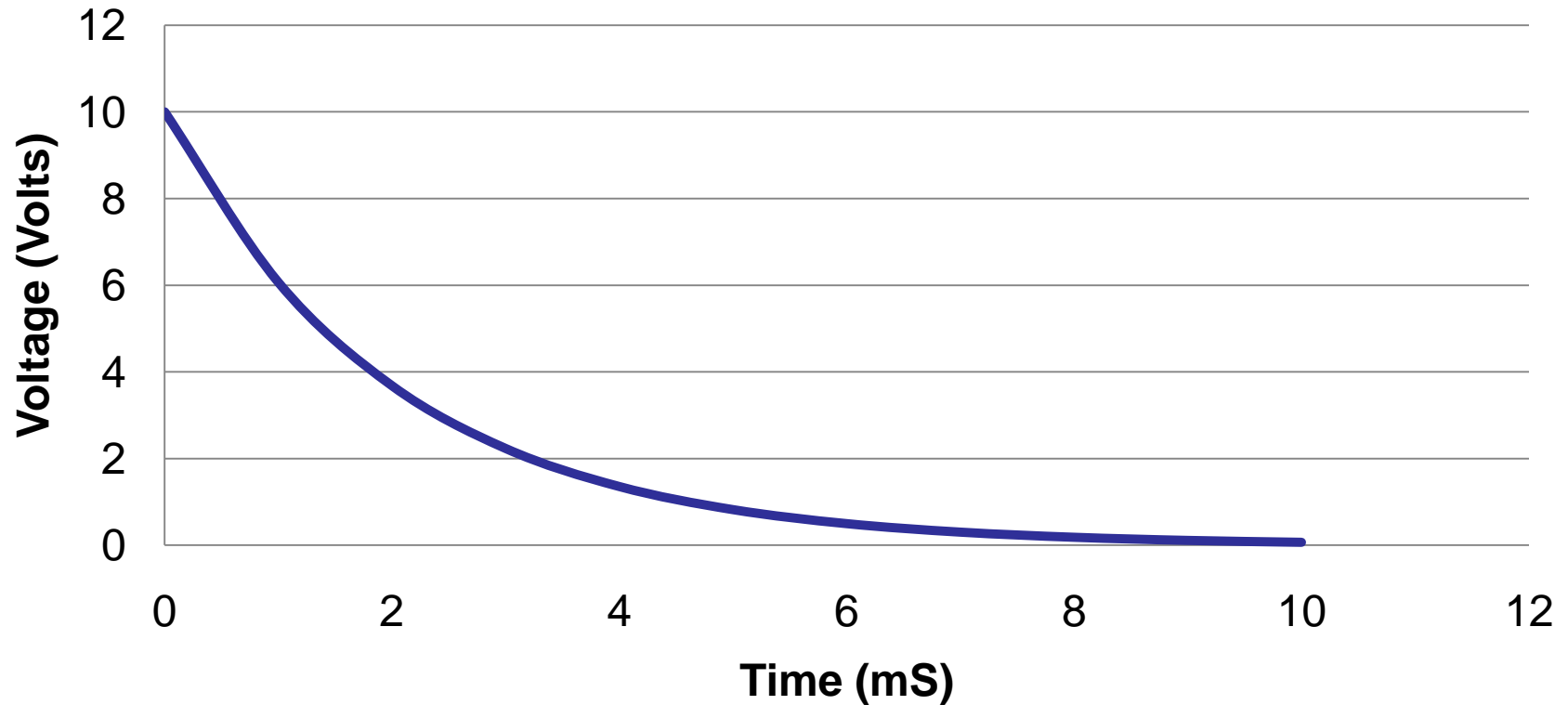

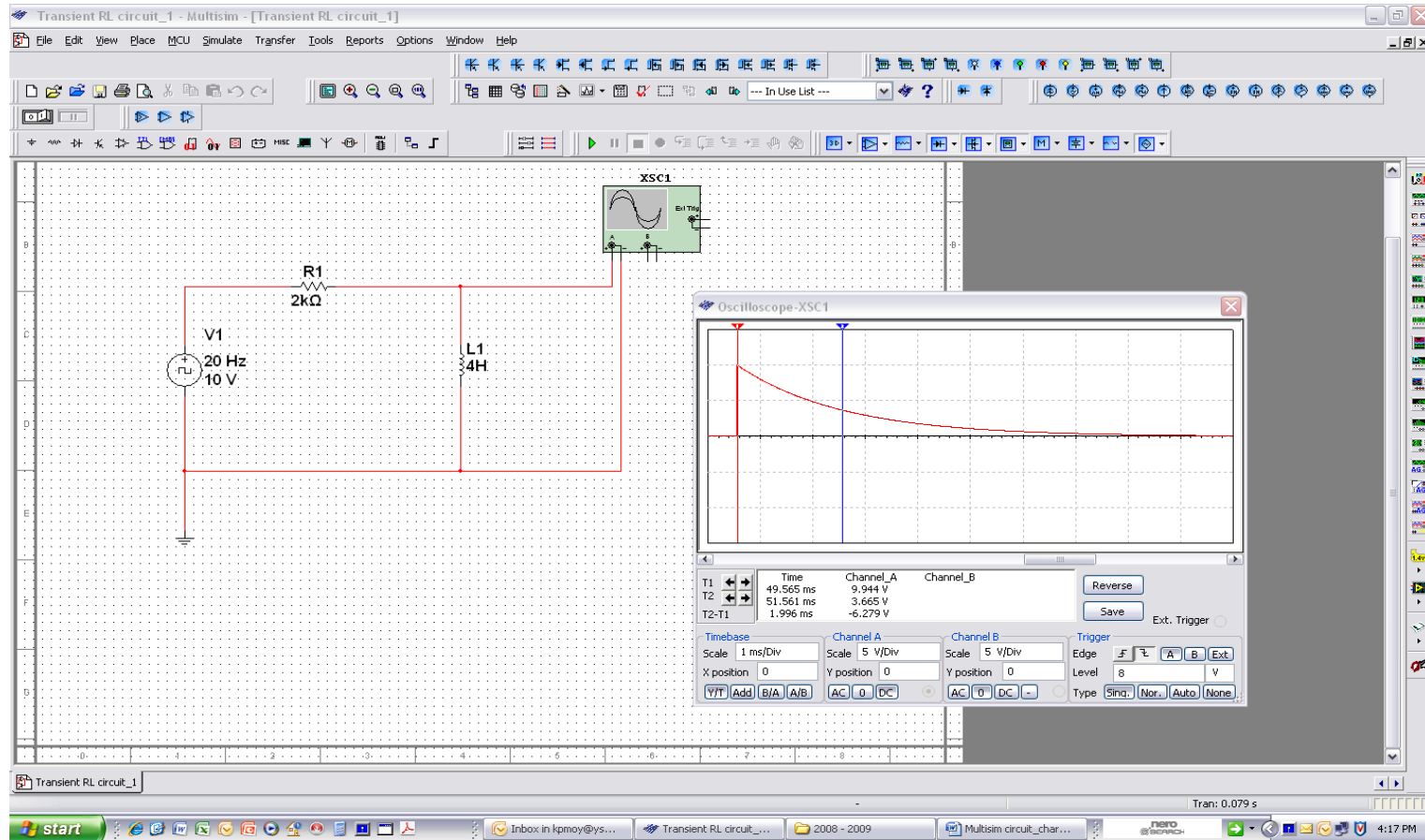
# Transient Voltage Simulation (Time Domain)– Multisim



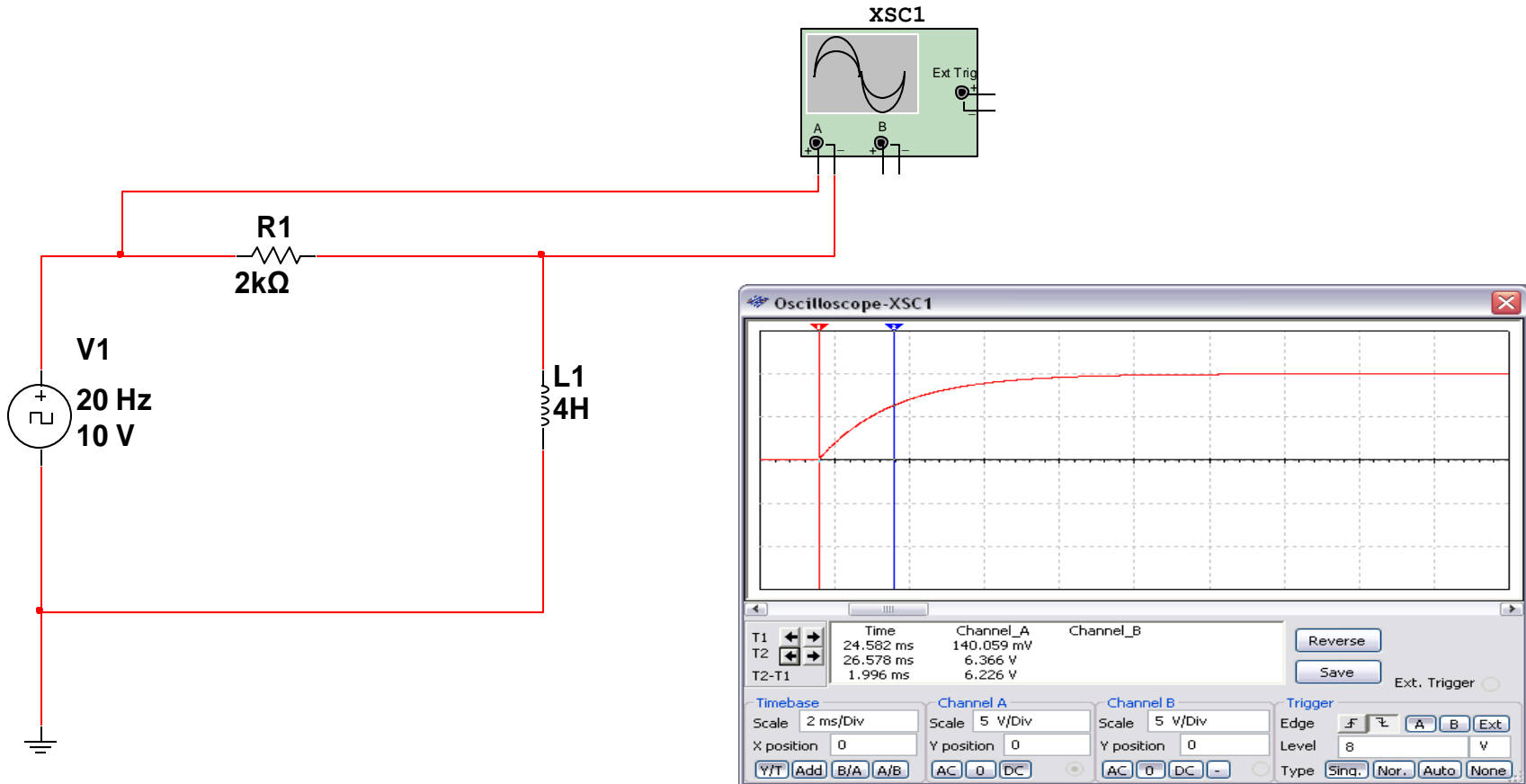
# Transient Current Simulation (Time Domain)– Multisim


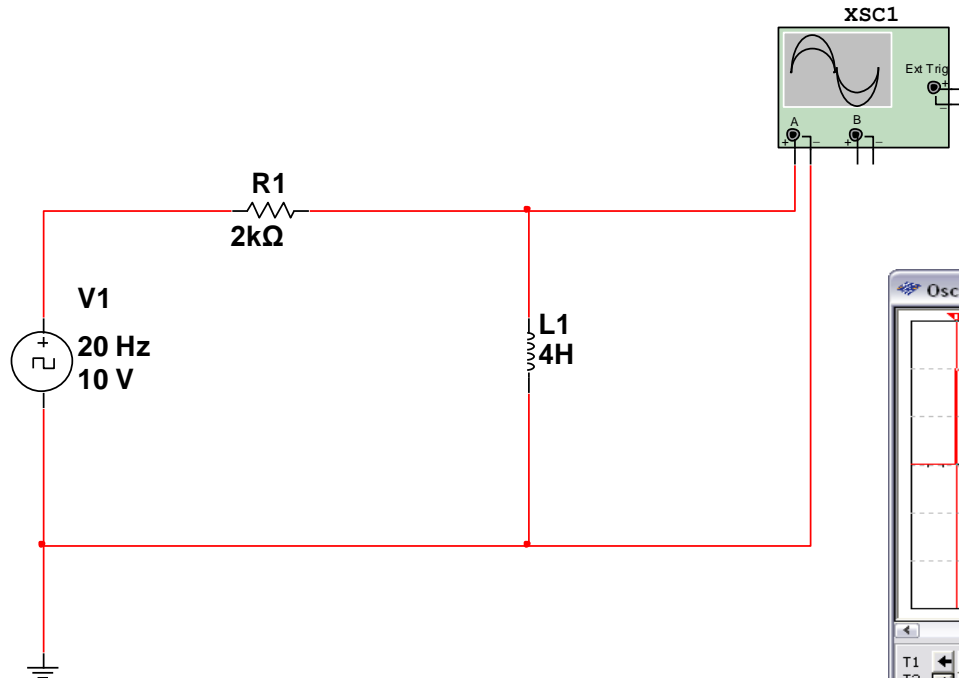
# Transient Voltage Simulation (Time Domain)– Multisim





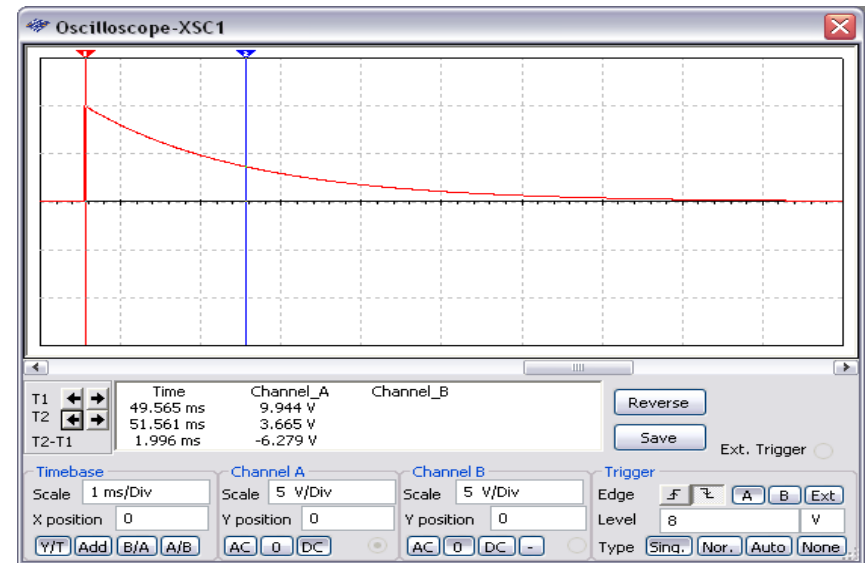Calculation:  
 $\tau = L/R = 4 \text{ H}/2\text{k}\Omega = 2 \text{ mS}$   
 $\tau(\text{calculated}) = 2 \text{ mS}$   
 $\tau(\text{measured}) = 1.996 \text{ mS}$




# Comparisons between Multisim and Excel Graphs

## Multisim

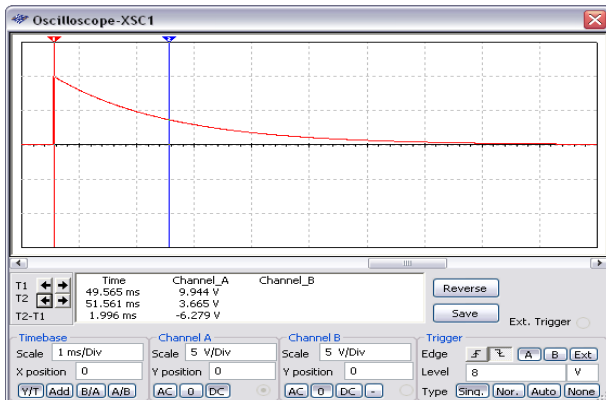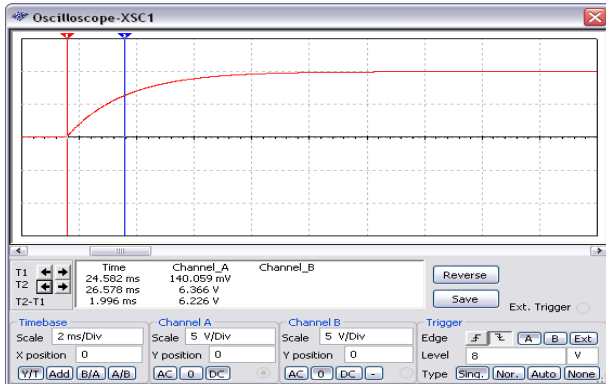


## Excel

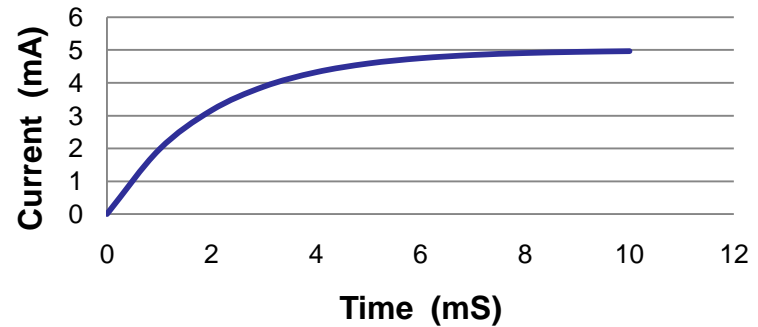**Transient Charging Current - Inductor**



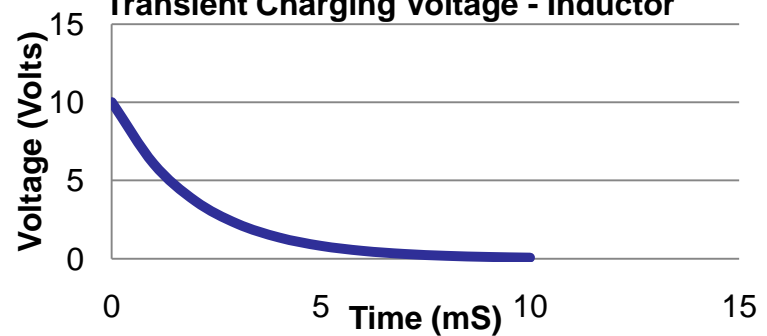**Transient Charging Voltage - Inductor**



## Summary

- Established RL circuit and develop differential equation for charging current and voltage for the inductor
- Utilized Laplace transform to change time domain differential equation into frequency domain equations
- Simplified equations using Partial Fraction
- Applied inverse Laplace Transform to covert equation back into time domain
- Developed current and voltage vs. time graph using Excel
- Performed circuit simulation (Multisim) to obtain time domain current and voltage graph
- Compare graphs developed by Multisim & Excel